

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4
5  -----
6  -- 7-segment display driver. It displays a 4-bit number on a 7-segment
7  -- This is created as an entity so that it can be reused many times easily
8  --
9
10 entity SevenSegment is port (
11     hex      : in  std_logic_vector(3 downto 0);  -- The 4 bit data to be displayed
12     sevensseg : out std_logic_vector(6 downto 0)    -- 7-bit outputs to a 7-segment
13 );
14 end SevenSegment;
15
16 architecture Behavioral of SevenSegment is
17
18     --
19     -- The following statements convert a 4-bit input, called dataIn to a pattern of 7 bits
20     -- The segment turns on when it is '1' otherwise '0'
21     --
22     begin
23         with hex select
24             sevensseg <=
25                 --GFEDCBA      3210      -- data in
26                 "0111111" when "0000", -- [0]
27                 "0000110" when "0001", -- [1]
28                 "1011011" when "0010", -- [2]
29                 "1001111" when "0011", -- [3]
30                 "1100110" when "0100", -- [4]
31                 "1101101" when "0101", -- [5]
32                 "1111101" when "0110", -- [6]
33                 "0000111" when "0111", -- [7]
34                 "1111111" when "1000", -- [8]
35                 "1101111" when "1001", -- [9]
36                 "1110111" when "1010", -- [A]
37                 "1111100" when "1011", -- [b]
38                 "1011000" when "1100", -- [c]
39                 "1011110" when "1101", -- [d]
40                 "1111001" when "1110", -- [E]
41                 "1110001" when "1111", -- [F]
42                 "0000000" when others; -- [ ]
43     end architecture Behavioral;
44     -----
45

```

