66 67

WHEN Extended =>

```
68
                    next_state <= Extended;</pre>
                    IF(Extend_tog='0') THEN
 69
 70
                       next_state <= Retracting; -- Here when the push button is presses, it would</pre>
      retract now
 71
                    END IF;
 72
73
74
75
76
                WHEN Retracting =>
                    next_state <= Retracting;
IF(leds = "0000")THEN
                       next_state <= Retracted; -- If all the leds are down, then that means the</pre>
      extender has retracted so we move to that state ELSIF (Extend_tog = '1') THEN
 77
 78
                       next_state <= Retracter_hold; -- Similarly if we release the button midway,</pre>
      it is now in hold state
 79
                       END IF;
 80
 81
                WHEN Retracter_hold =>
 82
                    next_state <= Retracter_hold;</pre>
 83
                    IF(Extend_tog='0') THEN
 84
                       next_state <= Retracting; -- If the button is pressed again, it should keep</pre>
      on retracting
 85
                       END IF;
 86
 87
                WHEN Retracted =>
      88
 89
 90
 91
                    END IF;
 92
             END CASE;
 93
       END PROCESS;
 94
 95

    DECODER SECTION PROCESS

 96
      Decoder_Section: PROCESS (current_state)
 97
 98
      BEGIN
 99
            CASE current_state IS
100
                WHEN Start =>
                shift_reg_en <= '0'; -- Everything should be 0 because we don't want to do anything
shift_reg_dir <= '0';</pre>
101
102
                Extender_out <= '0';
103
                Grappler_en <= '0';
104
105
106
                                       -- Here since leds should increase to the right,
                WHEN Extending =>
      shift_reg_dir is 1 along with enable and the extender will be out
                shift_reg_en <= '1';
shift_reg_dir <= '1'
Extender_out <= '1';
107
108
109
                Grappler_en <= '0':</pre>
110
111
                WHEN Extended => -- when it is extended, we can use the grappler, so
112
      grappler_en is 1
                shift_reg_en <= '0';</pre>
113
                shift_reg_dir <= '0';
Extender_out <= '1';
114
115
                Grappler_en <= '1';</pre>
116
117
                WHEN Retracting =>
                                         -- While retracting the leds will go down in the left
118
      direction so shhift_reg_dir is 0
                shift_reg_en <= '1';
119
                shift_reg_dir <= '0';
Extender_out <= '1';
120
121
                Grappler_en <= '0':</pre>
122
123
124
                                       -- after the extender has been retracted, everything should
                WHEN Retracted =>
      125
                shift_reg_dir <= '0'
126
                Extender_out <= '0';</pre>
127
128
                Grappler_en <= '0';
129
130
                WHEN others =>
                                      -- In all other cases, the extender will be open so its value
      is 1
                shift_reg_en <= '0';</pre>
131
                shift_reg_dir <= '0';
132
                Extender_out <= '1';</pre>
133
```