

```
1  library IEEE;
2  use IEEE.std_logic_1164.all;
3  use IEEE.numeric_std.all;
4
5  entity dwl is
6      port(
7          AGTB          : in std_logic; -- input (A>B) as obtained from the 4-bit comparator
8          AEQB          : in std_logic; -- input (A=B) as obtained from the 4-bit comparator
9          ALTB          : in std_logic; -- input (A<B) as obtained from the 4-bit comparator
10         door          : in std_logic; -- input from pb(0)
11         window        : in std_logic; -- input from pb(1)
12         leds_out       : out std_logic_vector(5 downto 0) -- output for the leds
13     );
14 end entity dwl;
15
16 architecture logic_dwl of dwl is
17 begin
18
19     leds_out(2) <= AGTB AND window AND door; -- If it's ABOVE temp and the window and door
20     are closed, the A/C should turn ON
21     leds_out(1) <= AEQB; -- If the current and desired temp are equal,
22     then system is AT temp
23     leds_out(0) <= ALTB AND window AND door; -- If it's BELOW temp and the window and door
24     are closed, the Furnace should turn ON
25     leds_out(3) <= (AGTB OR ALTB) AND window AND door; -- If A/C or Furnace is ON and the
26     door and window are closed
27     leds_out(4) <= NOT(door); -- when pb(0) is pressed, that means the door is open
28     leds_out(5) <= NOT(window); -- when pb(1) is pressed, that means the window is open
29 end logic_dwl;
```